



# Introduction to FPGA Design

## *Getting Started with Xilinx FPGAs Version 2.1i*

Intro to FPGA Design 6-1

© 1999 Xilinx, Inc.  
All Rights Reserved

No part of this document may be reproduced or transmitted without the  
express written permission of the Director of Xilinx Customer Education.



## Outline

- ◆ Hierarchical Design
- ➔ ◆ **Synchronous Design for Xilinx FPGAs**
- ◆ Summary

Intro to FPGA Design 6-9

© 1999 Xilinx, Inc.  
All Rights Reserved

No part of this document may be reproduced or transmitted without the  
express written permission of the Director of Xilinx Customer Education.



# Synchronous Design

- ◆ **Why Synchronous Design?**
- ◆ **Xilinx FPGA Design Tips**

## Why Synchronous Design?

- ◆ **Synchronous circuits are more reliable**
  - *Events are triggered by clock edges which occur at well-defined intervals*
  - *Outputs from one logic stage have a full clock cycle to propagate to the next stage*
    - Skew between data arrival times is tolerated within the same clock period
- ◆ **Asynchronous circuits are less reliable**
  - *A delay may need to be a specific amount (e.g. 12ns)*
  - *Multiple delays may need to hold a specific relationship (e.g. DATA arrives 5ns before SELECT)*

# Case Studies


- ◆ **The design I did two years ago no longer works. What did Xilinx change in their FPGAs?**
  - *SRAM process improvements and geometry shrinks increase speed*
  - *Normal variations between wafer lots*
- ◆ **My design was working, but I re-routed my FPGA and now my design fails. What is happening?**
  - *Logic placement has changed, which affects internal routing delays*
- ◆ **My design passes a back-annotated timing simulation but fails in circuit. Is the timing simulation accurate?**
  - *Yes, the simulation is accurate*
  - *Timing simulation uses worst-case delays*
  - *Actual board-level conditions are usually better*

# Design Tips


## Xilinx FPGA Design

- ◆ **Reduce clock skew**
- ◆ **Clock dividers**
- ◆ **Avoid glitches on clocks and asynchronous set/reset signals**
- ◆ **The Global Set/Reset network**
- ◆ **Select a state machine encoding scheme**
- ◆ **Access carry logic**
- ◆ **Build efficient counters**

# Clock Skew

 

 - ◆ **This shift register will not work because of clock skew!**



© 1999 Xilinx, Inc.  
All Rights Reserved

Intro to FPGA Design 6-14

No part of this document may be reproduced or transmitted without the express written permission of the Director of Xilinx Customer Education.



# Use Global Buffers to Reduce Clock Skew

- ◆ **Global buffers are connected to dedicated routing**
  - *This routing network is balanced to minimize skew*
- ◆ **All Xilinx FPGAs have global buffers**
- ◆ **Different types of global buffers**
  - *XC4000E/L and Spartan have 4 BUFGPs and 4 BUFGSSs*
  - *XC4000EX/XL/XV have 8 BUFGGLSs*
  - *Virtex has 4 BUFGs or BUFGDLLs*
- ◆ **You can always use a BUFG symbol and the software will choose an appropriate buffer type**
  - *Most synthesis tools can infer global buffers onto clock signals*

© 1999 Xilinx, Inc.  
All Rights Reserved

Intro to FPGA Design 6-15


No part of this document may be reproduced or transmitted without the express written permission of the Director of Xilinx Customer Education.




 
# Traditional Clock Divider

- ◆ Introduces clock skew between CLK1 and CLK2
- ◆ Uses an extra BUFG to reduce skew on CLK2



© 1999 Xilinx, Inc.  
All Rights Reserved


Intro to FPGA Design 6-16

*No part of this document may be reproduced or transmitted without the express written permission of the Director of Xilinx Customer Education.*



# Recommended Clock Divider

- ◆ No clock skew between flip-flops

 

© 1999 Xilinx, Inc.  
All Rights Reserved


Intro to FPGA Design 6-17

*No part of this document may be reproduced or transmitted without the express written permission of the Director of Xilinx Customer Education.*


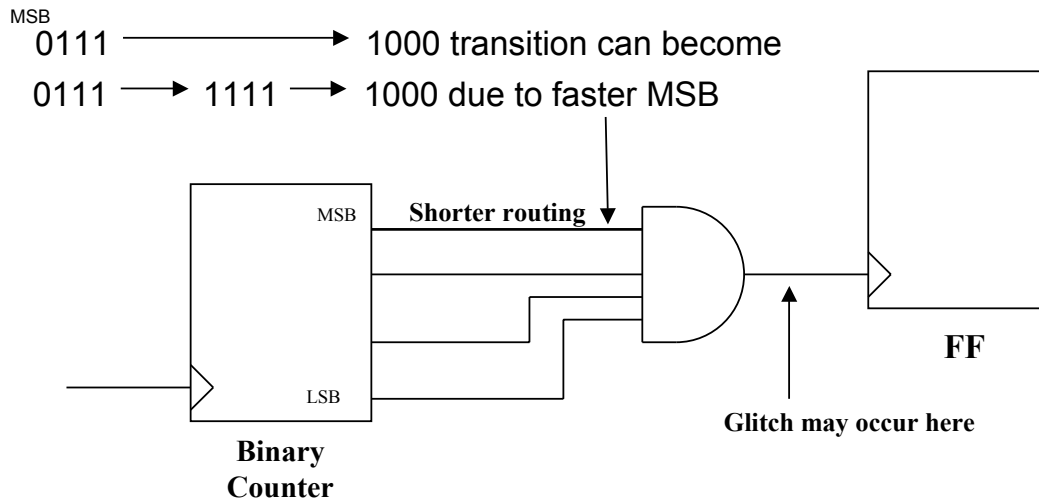
# Avoid Clock Glitches

- ◆ Because flip-flops in today's FPGAs are very fast, they can respond to very narrow clock pulses
- ◆ Never source a clock signal from combinatorial logic
  - Also known as “gating the clock”



© 1999 Xilinx, Inc.  
All Rights Reserved


Intro to FPGA Design 6-18

No part of this document may be reproduced or transmitted without the express written permission of the Director of Xilinx Customer Education.


 
# Avoid Clock Glitches: Answer

- ◆ Complete in the circuit to create the same function, but without glitches on the clock



© 1999 Xilinx, Inc.  
All Rights Reserved


Intro to FPGA Design 6-21

No part of this document may be reproduced or transmitted without the express written permission of the Director of Xilinx Customer Education.


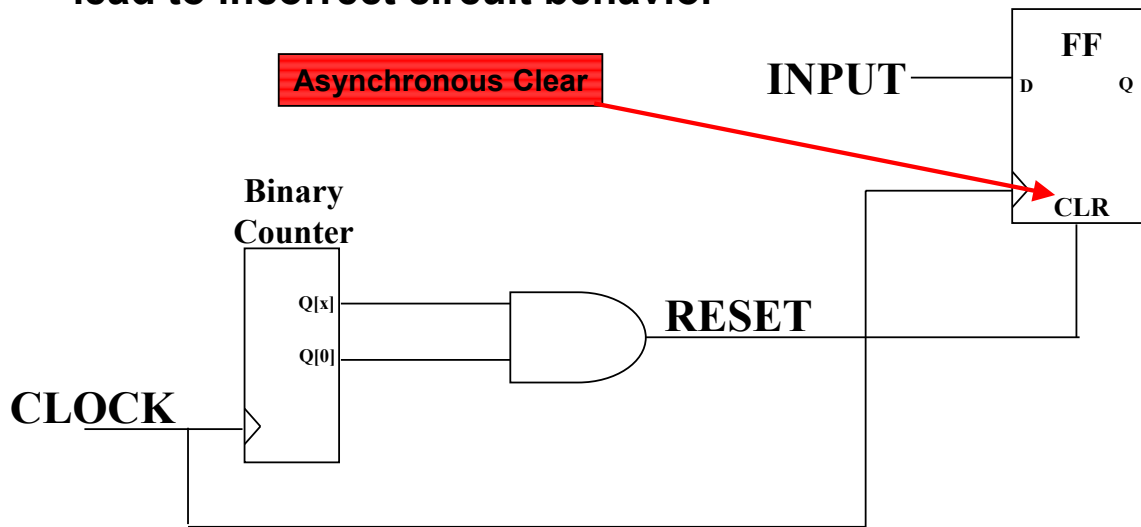
# Avoid Set/Reset Glitches

- ◆ Glitches on asynchronous clear or preset inputs can lead to incorrect circuit behavior



© 1999 Xilinx, Inc.  
All Rights Reserved


Intro to FPGA Design 6-22

No part of this document may be reproduced or transmitted without the express written permission of the Director of Xilinx Customer Education.


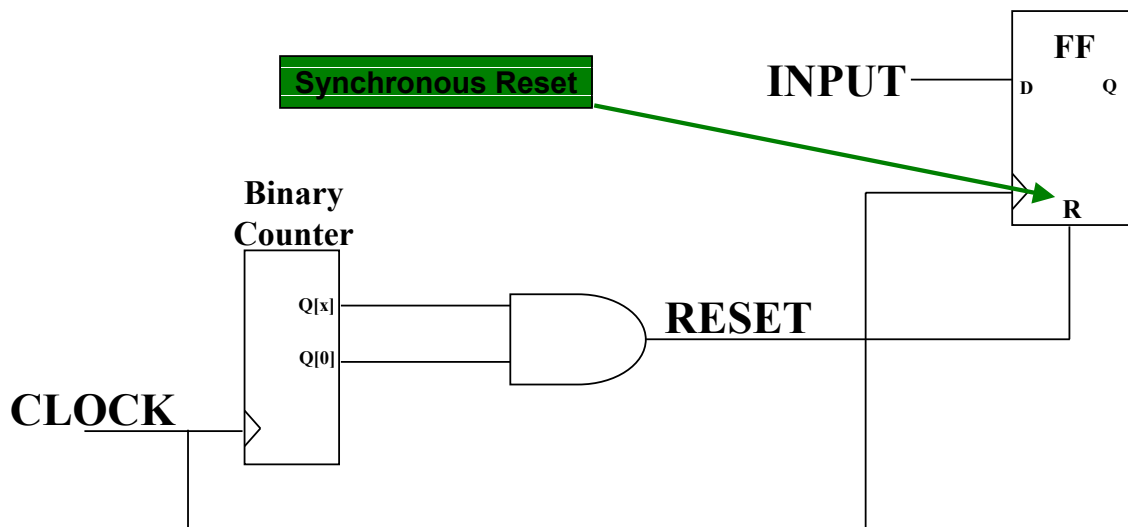
# Avoid Set/Reset Glitches

- ◆ Convert to synchronous set or reset when possible



© 1999 Xilinx, Inc.  
All Rights Reserved

Intro to FPGA Design 6-23

No part of this document may be reproduced or transmitted without the express written permission of the Director of Xilinx Customer Education.

